



**MANIPAL**  
ACADEMY of HIGHER EDUCATION  
*(Institution of Eminence Deemed to be University)*

**DEPARTMENT OF ELECTRONICS AND COMMUNICATION  
ENGINEERING  
M.TECH in ELECTRONICS ENGINEERING (MICROELECTRONICS)**

**ANALOG and RF (ECE 5117)**

**Assignment 2:**

**DESIGN OF TWO STAGE OPAM USING 90nm CMOS technology**

Submitted by

**Gagan R (251090420018)**

Under the Guidance of:

**Dr. Sunil Rathore**

## Abstract:

This report presents the design of a two-stage CMOS operational amplifier (op-amp) targeted for a 90 nm CMOS process. The design focuses on achieving high DC gain, adequate bandwidth, stable frequency response with Miller compensation, controlled slew rate, and reasonable power consumption for typical analog integrated circuit applications (e.g., ADC front-ends, comparators, and amplifiers).

## Objective:

The objective of this project was to design a robust two-stage Operational Transconductance Amplifier (OTA) in 90 nm CMOS technology, calculate the dimensions (W/L ratios) and bias currents for all transistors, and verify the resulting Total DC Voltage Gain ( $A_v$ ).

## Theory and Design Parameters:

The OTA employs a standard two-stage architecture: a **NMOS input differential pair** (M1-M2) with PMOS current mirror loads (M3-M4) for the first stage, followed by an **PMOS common-source stage** (M6) with a PMOS current source load (M7) for the second stage. Miller compensation ( $c = 800$  fF) is applied between the two stages to ensure stability.

## Block Diagram:

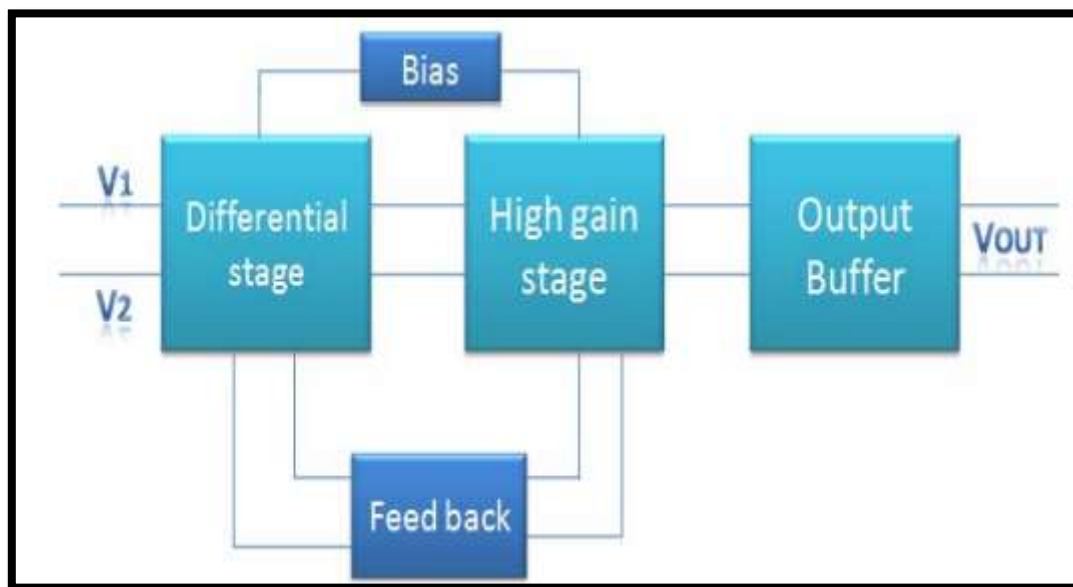



Figure 1: Block Diagram




## Calculations and Results:

The final design parameters, including the theoretically calculated W/L ratios and final bias currents, are summarized below:

### PMOS TEST:

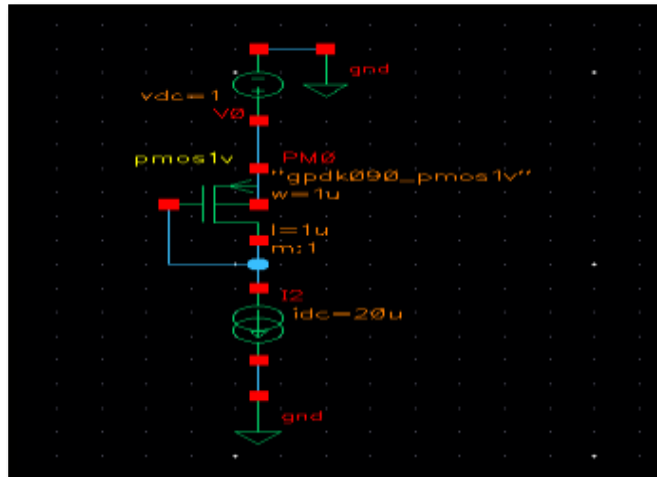

### NMOS TEST:

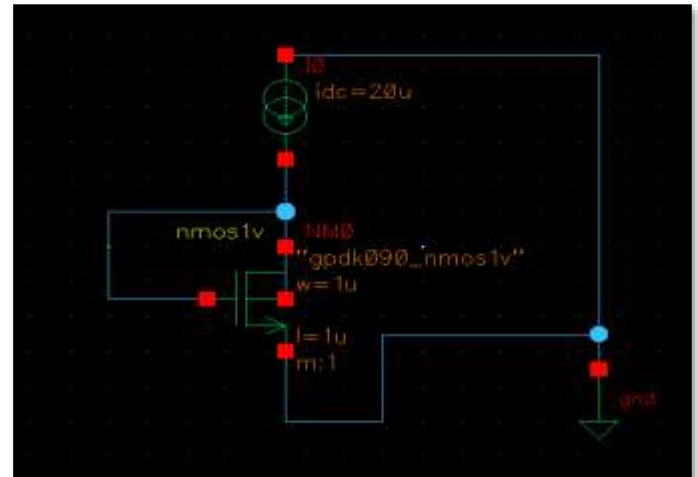

### VTHP BETAEFF

Window	Expressions	Info	Help
signal	OP("/PM0" "??")		
Iavl	NaN		
beff	139.249u		
betaeff	208.479u		
cbb	111.222a		

### NMOS BETAEFF

Window	Expressions	Info	Help
signal	OP("/NM0" "??")		
Iavl	NaN		
beff	245.509u		
betaeff	300.632u		
cbb	111.222a		

### Vthp 1.6 V

vgs	-271.50m
vgsteff	15.1258m
vgt	24.1287m
vsat_marg	-217.625m
vsb	-0
vth	-295.689m
vth0	NaN
vth drive	NaN

### Vthn 1.6 V; ICMR+

vgt	92.9595m
vsat_marg	240.674m
vsb	1.18409
vth	322.947m

### Vthp 800m

vgs	-271.604m
vgd	0
vgs	-271.604m
vgsteff	15.1407m
vgt	24.082m
vsat_marg	-217.656m
vsb	-0
vth	-295.686m

### Vthn 800m

vgs	84.8514m
vsat_marg	903.134m
vsb	530.456m
vth	184.712m

### VTHN differial test

vgs	518.254m
vgsteff	391.366m
vgt	397.489m
vsat_marg	192.11m
vsb	-518.254m
vth	120.765m

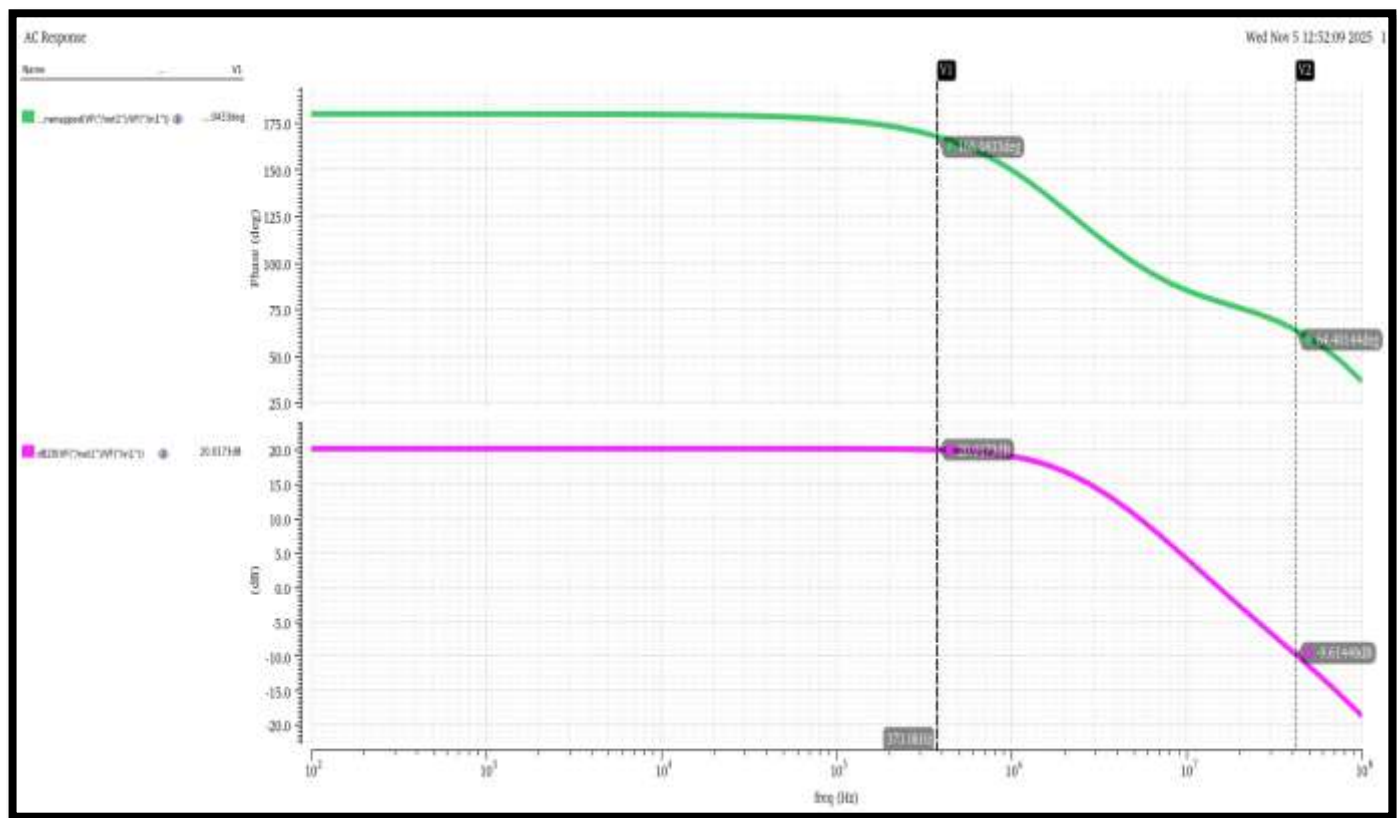


Figure 4: Gain bandwidth Phase Margin with 1.6V

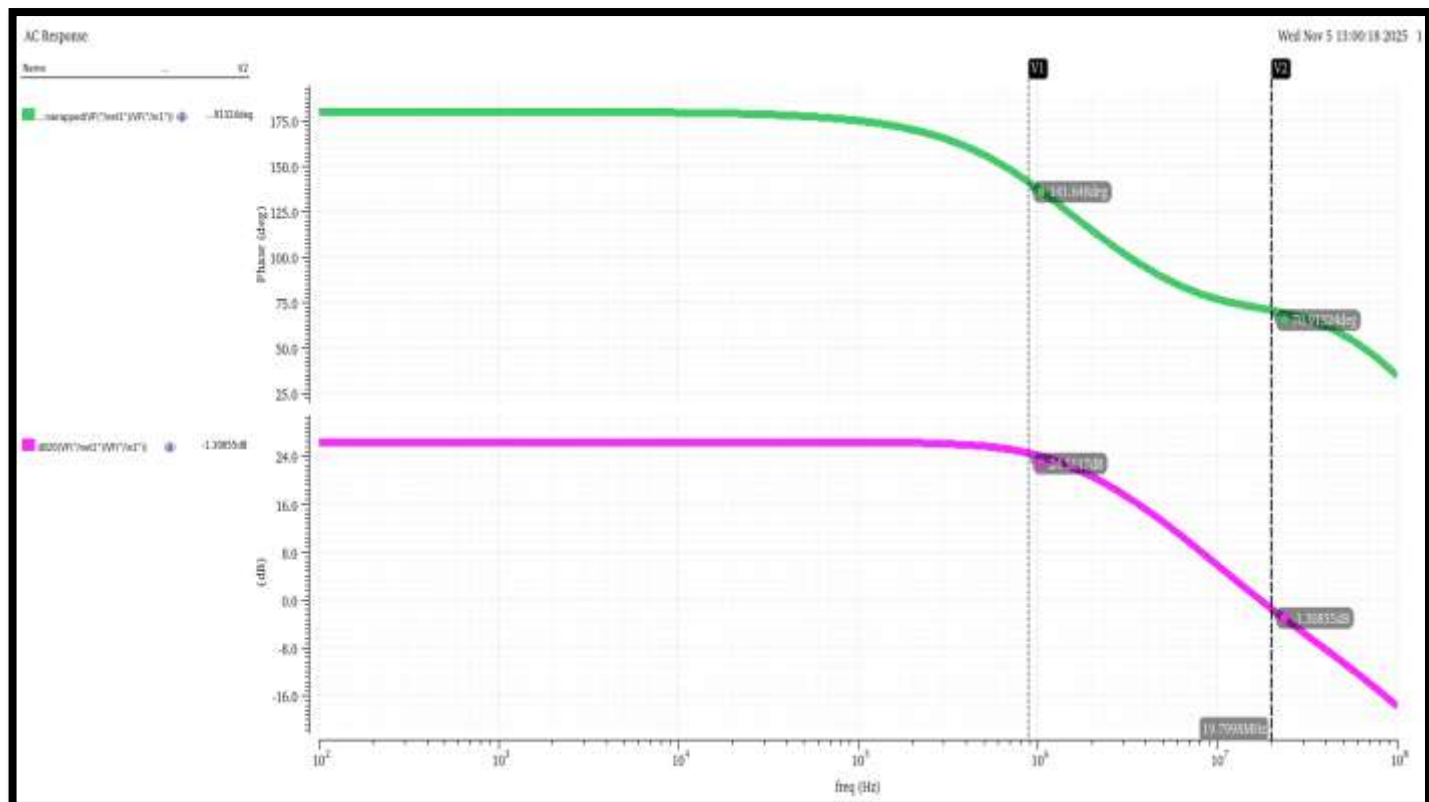


Figure 5: Gain bandwidth Phase Margin with 800 mV

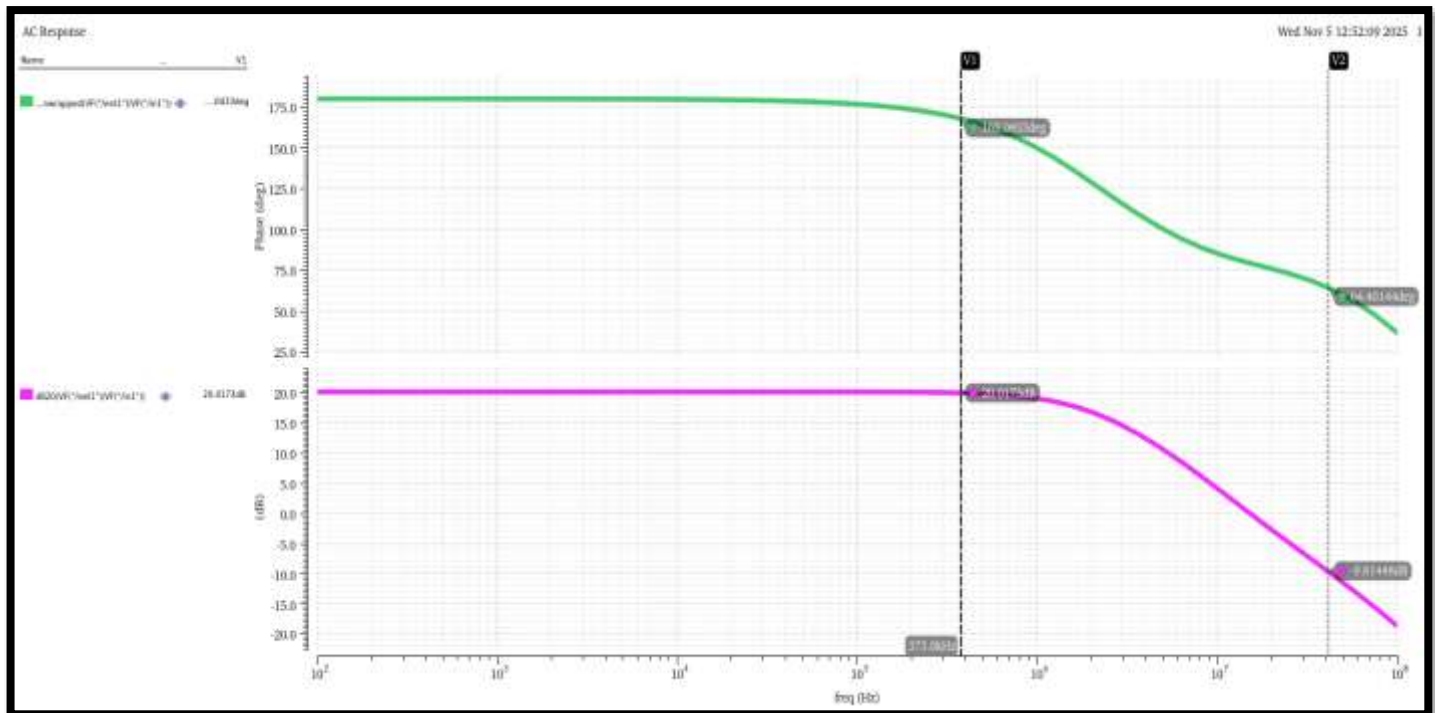


Figure 6: Gain bandwidth Phase Margin with 1.2V

	Name	Value
1	:pwr	541.1E-6
2	NM1:pwr	7.651E-6
3	NM2:pwr	7.604E-6
4	NM4:pwr	9.851E-6
5	NM5:pwr	11.43E-6
6	NM6:pwr	140.4E-6
7	PM1:pwr	5.348E-6
8	PM3:pwr	5.332E-6
9	PM4:pwr	353.5E-6
10	0/0/PLUS	214.35E-6

:pwr(W)=0.00054107608  
NM1:pwr(W)=7.6514414e-06  
NM2:pwr(W)=7.6036072e-06  
NM4:pwr(W)=9.8511777e-06  
NM5:pwr(W)=1.1432547e-05  
NM6:pwr(W)=0.0001403929  
PM1:pwr(W)=5.347841e-06  
PM3:pwr(W)=5.3316341e-06  
PM4:pwr(W)=0.00035346493

Figure 8: Total Power View with 800 mV

## Conclusion:

Table 1: Theoretically calculated values

Parameter	Device/Stage	Theoretical Calculated Value	Units
Input W/L	$M_{1,2}$ (NMOS Differential Pair)	<b>4.27</b>	Ratio
Current Mirror W/L	$M_{3,4}$ (PMOS Load)	<b>0.139</b>	Ratio
Second Stage Driver W/L	$M_6$ (PMOS Driver)	<b>29.62</b>	Ratio
Output Load W/L	$M_7$ (NMOS Load)	<b>15.0</b>	Ratio
First Stage Bias Current	$I_4$	$10\mu\text{A}$	$\mu\text{A}$
Second Stage Bias Current	$I_6 = I_7$	$300\mu\text{A}$	$\mu\text{A}$
First Stage Gain ( $A_{v1}$ )	$\frac{g_{m1}}{g_{ds2} + g_{ds4}}$	<b>3.01</b> (9.544 dB)	V/V (dB)
Second Stage Gain ( $A_{v2}$ )	$\frac{g_{m6}}{g_{ds6} + g_{ds7}}$	<b>3.403</b> (10.63 dB)	V/V (dB)
Total DC Gain	$A_{v1} + A_{v2}$ (in dB)	<b>20.17 dB</b>	dB

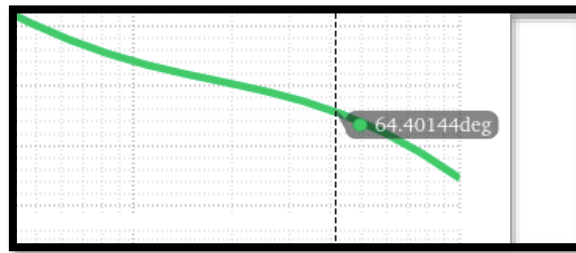


Figure 9: observed Phase Margin

Table 2: Comparison Table

Parameter	Theoretical	Practical Results
DC Gain	20.17dB	24.57 dB (low due to device sizing)
PhaseMargin	64.401deg	64° (stable operation)
Power	571.6 $\mu\text{W}$ (total)	541.1 $\mu\text{W}$ (total)



# Design of Two stage 90nm

1)  $C_C = 800 \text{ fF}$

$I_5 = 20 \mu\text{A}$

$g_{m1} = 160 \mu$

$\beta_{effp} = 142.924 \mu$

$\beta_{effn} = 300.632 \mu$

a)  $m1 \& m2$

$$\left(\frac{W}{L}\right)_1 = \frac{g_{m1}^2}{\mu_n C_{ox} (2I_{D1})}$$

$$= \frac{(160 \mu)^2}{(300.67 \mu) (20 \mu)}$$

$\left(\frac{W}{L}\right)_1 = 4.266$

$\left(\frac{W}{L}\right)_{1,2} \approx 5$

b)  $m3 \& m4$

$$\left(\frac{W}{L}\right)_3 = \frac{2I_{D3}}{\mu_p C_{ox} [V_{DD} - 1\text{CMR} - V_{t3\text{max}} - V_{t1\text{min}}]^2}$$

$= \frac{2(10 \mu)}{145 \mu [1.8 - 1.6 -$

$\left(\frac{W}{L}\right)_{3,4} = \frac{2(10 \mu)}{143 \mu [1.8 - 1.6 - (0.295 \times 10^{-3}) + 0.184]^2}$   $\frac{W}{L} = 5$   
 $= 5 \times 1000$

$\left(\frac{W}{L}\right)_{(3,4)} = 0.139 \approx 1$   $W = L$

$\frac{2.5}{500} = 5$

$V_{DSat} \geq 1\text{CMR} - \sqrt{\frac{2I_{D1}}{\beta_1}} - V_{t1\text{max}}$

$0.8 - \sqrt{\frac{2(10 \mu)}{(300 \mu) 5}} - 0.322$

$= 0.8 - 0.1154 - 0.322$

$= 0.3626$

$V_{DSat} = 362 \text{ mV}$

$0.295 \uparrow$   
 $95 \mu\text{V}$

362 mV

$V_{th1} = 322.947 \text{ mV}$   
 $n_{\text{max}}$

$V_{th1} = 184.71 \text{ mV}$   
 $n_{\text{min}}$

$V_{th3} = -295 \text{ mV}$   
 $n_{\text{max, min}}$



$$e) g_{m6} \geq 1600 \mu$$

$$\left(\frac{W}{L}\right)_4 = 1 \quad \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4} = \frac{g_{m6}}{g_{m4}}$$

$$g_{m4} = \sqrt{4\mu C_{ox} \left(\frac{W}{L}\right)_4 2I_D}$$

$$= \sqrt{143 (1) 20}$$

$$g_{m4} = 53.47 \mu$$

$$g) \left(\frac{W}{L}\right)_6 = \frac{g_{m6}}{g_{m4}} \left(\frac{W}{L}\right)_4$$

$$= \frac{1600 \mu}{54 \mu} (1)$$

$$\left(\frac{W}{L}\right)_6 = 29.62$$

$$h) \frac{I_6}{I_4} = \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4} = \frac{30}{1}$$

$$I_6 = 30(I_4) = 30(10) = 300 \mu A$$

$$\boxed{I_6 = 300 \mu A}$$

$$I_6 = 47$$

$$i) \frac{I_7}{I_5} = \frac{\left(\frac{W}{L}\right)_7}{\left(\frac{W}{L}\right)_5} \Rightarrow \left(\frac{W}{L}\right)_7 = \left(\frac{I_7}{I_5}\right) \left(\frac{W}{L}\right)_5$$

$$= \frac{300}{20} (1)$$

$$\boxed{\left(\frac{W}{L}\right)_7 = 15}$$

$$f) = 2 I_{D5} / \mu_n C_{ox} (V_{DSat})^2$$

$$\left(\frac{W}{L}\right)_5 = \frac{2(20 \mu)}{300 (362 m)^2}$$

$$= \frac{40 \mu}{300 [0.131044]}$$

$$\left(\frac{W}{L}\right)_5 = 1.017$$

$$\boxed{\left(\frac{W}{L}\right)_5 = 1}$$

→ From Calculations :-

I got

$$I_5 = 20 \mu$$

$$C_C = 800 \text{ fF}$$

$$m_1, m_2 = 5 \Rightarrow \left(\frac{W}{L}\right)_{2,1} = \frac{0.5 \mu}{100 \text{ n}}$$

$$m_3, m_4 = 1 \Rightarrow \left(\frac{W}{L}\right)_{3,4} = \frac{1 \mu}{1 \mu}$$

$$m_6 = 30 \Rightarrow \left(\frac{W}{L}\right)_6 = \frac{3 \mu}{100 \text{ n}}$$

$$m_7 = 15 \Rightarrow \left(\frac{W}{L}\right)_7 = \frac{1.5 \mu}{100 \text{ n}}$$

$$I_6, I_7 = 300 \mu$$

from above values, it is found that all mosfets are in Saturation

→ To calculate gain in each stage

$$1^{\text{st}} \text{ stage: } A_{v1} = g_{m1} (r_{o1} || r_{o4})$$

$$A_{v1} \propto (m_1 \& m_2) \uparrow \quad g_{m1} \uparrow$$

$$\therefore g_{m1} = 145.46 \mu$$

$$g_{ds1} = 48.065 \mu$$

$$g_{ds4} = 256.478 \text{ n}$$

2<sup>nd</sup> stage

$$g_{m6} = 1.31 \text{ m}$$

$$g_{ds6} = 162.591 \mu$$

$$g_{ds7} = 222.29 \mu$$

I<sup>st</sup>  
stage

$$\text{Gain} = \frac{g_{m1}}{g_{ds1} + g_{ds4}} = \frac{145.46 \mu}{48.065 \mu + 256.478 \mu}$$

$$= 3.01$$

$$\boxed{\text{gain(dB)} = 9.544}$$

II<sup>nd</sup>  
stage

$$\text{Gain} = \frac{1310}{162.53 + 222.23} = 3.403$$

$$\text{gain(dB)} = 10.63$$

$$\boxed{\text{Total gain} = 20.17}$$

Total Power dissipation:-

$$P = V I_{\text{all current}}$$

$$= V_{DD} I_{\text{current through all MOSFETs}}$$

$$= (1.8)(300 \mu + 20 \mu)$$

$$\boxed{P = 576 \mu W}$$



Design

# Two Stage opAMP :-

$$DC \text{ Gain} = 1000 = 20 \log(100) = 60 \text{ dB}$$

$$GBW = 30 \text{ MHz}$$

$$PM \geq 60^\circ$$

$$\text{Slew rate} = 20 \text{ V/}\mu\text{sec}$$

$$ICMR(+) = 1.6 \text{ V}$$


$$ICMR(-) = 0.8 \text{ V}$$

$$C_L = 2 \text{ pF}$$

$$V_{DD} = 1.8 \text{ V}$$

$$\text{Process} = 180 \text{ nm}$$

$$\text{Power} \leq 300 \mu\text{W}$$

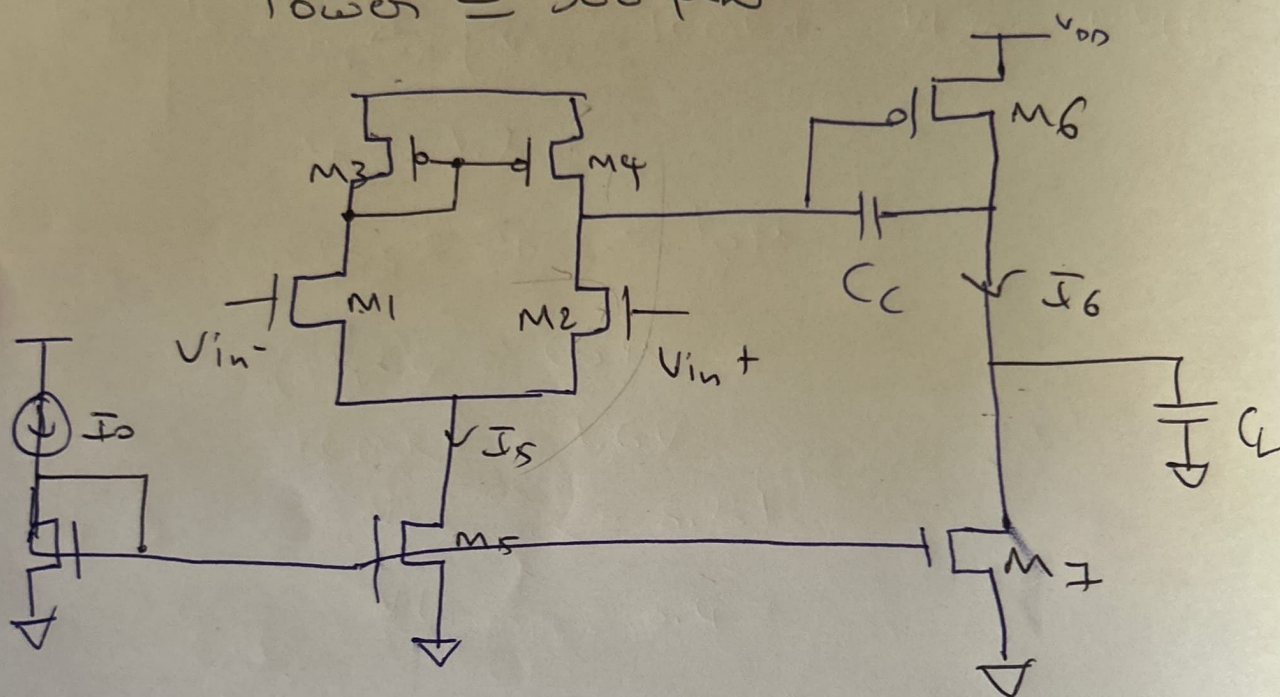

$m3 \ \& \ m4$  from  $\rightarrow ICMR^+$

$m1 \ \& \ m2 \rightarrow GBW$

$I_5 \rightarrow \text{Slew rate}$

$m7 \leftrightarrow m5 \rightarrow ICMR^- \text{ (min)}$

$M_6$  from gain

$C_c \rightarrow \text{Phase margin}$

$$\text{beta}_{eff} = \frac{g_m C_{ox} W}{g_m C_{ox} L}$$



$$① L = 500nm$$

$$② C_c \geq 0.22 C_L$$

$$C_c \geq 0.22 \times 20F$$

$$C_c \geq 0.44 pF$$

$$\geq 440 pF \text{ about}$$

$$C_c = 800 pF$$

$$③ \text{ from GBW: } M1 \& M2?$$


$$g_{m1} = g_B \times C_c \times 2\pi$$

$$= 30MHz \times 800 pF \times 2\pi$$

$$g_{m1} = 150.79 \mu$$

$$g_{m1} = 160 \mu$$
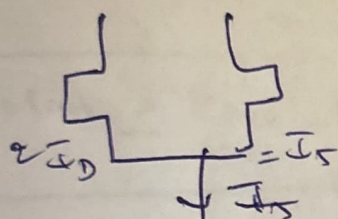
$$\left(\frac{W}{L}\right) = \frac{g_m^2}{\mu_n C_{ox} \cdot 2\bar{I}_D}$$



$$2\bar{I}_D = \bar{I}_S$$

$$\bar{I}_D = \frac{\bar{I}_S}{2}$$

$$\left(\frac{W}{L}\right)_1 = \frac{g_{m1}^2}{\mu_n C_{ox} (2\bar{I}_{D1})}$$

$$= \frac{g_{m1}^2}{\mu_n C_{ox} \bar{I}_S}$$

$$= \frac{160^2}{300 \times 20} = 4.266$$

$$\therefore \left(\frac{W}{L}\right)_{1,2} = 5$$

$$③ \text{ Slew rate: } \frac{\bar{I}_S}{C_c}?$$


$$\bar{I}_S = SR \cdot C_c$$

$$= \frac{20 V}{ms} \cdot 800 pF$$

$$= 16 \mu A$$

$$\bar{I}_S = 20 \mu A$$

$$④ M3 \& M4$$

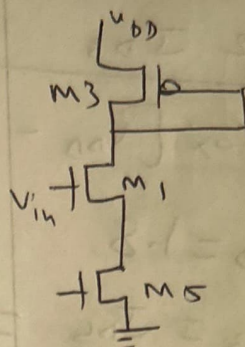

M3 is always saturation


$V_{in} \uparrow$  M1  $\rightarrow$  triode

$$V_D > V_G - V_{tM1}$$

$$V_G < V_D + V_{t1}$$

$$V_{in} < V_{D1} + V_{t1}$$
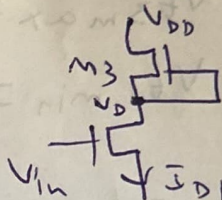
$$V_{inmax} = V_{D1} + V_{t1} \rightarrow ①$$



$$V_D = V_{DD} - V_{GS3}$$

$$\bar{I}_3 = \frac{\mu_p C_{ox} W}{2L} (V_G - V_{t3})^2$$

$$\bar{I}_3 = \frac{P}{2} (V_{GS} - V_t)^2$$

$$V_{GS3} = \sqrt{\frac{2\bar{I}_3}{\mu_p}} + |V_{t3}|$$

$$V_{D1} = V_{DD} - V_{GS3}$$

$$V_{D1} = V_{DD} - \left[ \sqrt{\frac{2\bar{I}_3}{\mu_p}} + |V_{t3}| \right]$$

$$V_{inmax} \leq V_{D1} + V_{t1}$$

$$\leq V_{DD} - \sqrt{\frac{2\bar{I}_{D3}}{\mu_p}} - |V_{t3}|_{max} + V_{t1min}$$

$$ICMR+ \leq V_{D1min} + V_{t1min}$$



$$\boxed{\begin{aligned}\mu_p \text{ Cox} &= 60 \mu \\ \mu_n \text{ Cox} &= 300 \mu\end{aligned}}$$

$$\frac{2\bar{I}_3}{\beta_3} = \left[ V_{DD} - I_{CMR_{\max}} - (V_{t3})_{\max} + V_{t1_{\min}} \right]^2$$

$$\frac{2\bar{I}_D}{\mu_p \text{ Cox} \left( \frac{W}{L} \right)_3} = V_{DD} - I_{CMR} - (V_{t3})_{\max} + V_{t1_{\min}}$$

$$\left( \frac{W}{L} \right)_3 = \frac{2\bar{I}_D}{\mu_p \text{ Cox} \left[ V_{DD} - I_{CMR} - (V_{t3})_{\max} + V_{t1_{\min}} \right]^2}$$

$$V_{DD} = 1.8$$

$$\bar{I}_D = \frac{\bar{I}_{DS}}{2} = 10 \mu$$

$$\mu_p \text{ Cox} = 60 \mu$$

$$I_{CMR} = 1.6 \text{ V}$$

$$V_{t3_{\max}} = 0.51$$


$$V_{t1_{\min}} = 0.47$$

$$= \frac{2(10 \mu)}{60 \mu [1.8 - 1.6 - 0.51 + 0.47]^2}$$

$$\boxed{\left( \frac{W}{L} \right)_{3,4} = 13.02 \approx 14}$$



⑤ Design for m5 :-

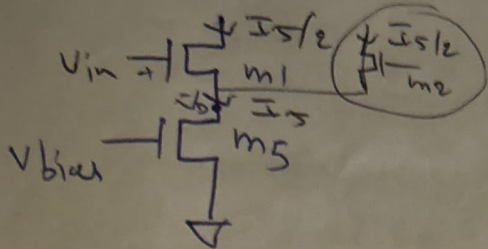

$$V_{in} \geq V_{gs1} + V_{D_{sect5}}$$

(min)  $N_5$  in next

$$V_{CMR - ve} \rightarrow V_{GS1} + V_{DSat}$$

$$I_{CMR} = \frac{1}{2} \left[ \sqrt{\frac{2I_0}{\beta_1}} + V_{t1} \right]_{\max} + V_{DSat}$$

$$I_{CMR} = \frac{I}{2} \sqrt{\frac{2I_{D1}}{\beta_1}} + V_{t_{max}} + V_{D_{sat}}$$

$$V_{DSsat} > \frac{V_{DD}}{2} - \sqrt{\frac{2I_{D1}}{\beta_1}} - V_{t1} \quad \text{max}$$

$$\gamma_{0.8} = \frac{\sqrt{2 \times (10 \mu)}}{\sqrt{300 \mu (5)}} = V_{t1 \max}$$

$$V_{\text{gsat}} = 0.8 - 0.115 \cdot 4 = 0.59 \text{ V}$$

$$= 94.6 \text{ mV}$$

$$\binom{7}{2}_5 = 6^4$$

$$V_{DSat} = 0.8 - \sqrt{\frac{2(10\mu)}{300\mu(6)}} - 0.59$$

$$= 105\text{mV}$$

$$I_{DS} = \frac{\mu_n C_{ox} \left( \frac{W}{L} \right)_S [V_{DSsat}]^2}{2}$$

$$\left(\frac{L}{L}\right)_5 = \frac{2505}{\mu_{nCOX}(V_{DSAT})^2}$$

$$= \frac{2(20\mu)}{300 \times (105\text{mV})^2} = 12.05$$

$$\left(\frac{w}{c}\right)_5 = 1d$$

$$\left(\frac{W}{C}\right)_{1,2} = 6$$

within Vin ↓

50 2 .

$$v_{D5} > v_g - v_t$$

$\therefore m_5$  goes to trade region


⑥ Design for M6

for 60° PM

$$g_{m,2} \geq 10 \cdot g_{m,1}$$

$$\geq 10 (160 \mu)$$

$$m_f \geq 1600 \mu$$

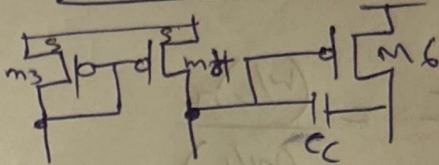

$v_{d3} \propto m_3 \text{ \& } m_4 \therefore v_{d3} \propto v_{d4}$

$$V_{DS} = V_{DS} = V_{DS}$$

$$V_{GS_{m3}} = V_{GS_{m4}} = V_{GS_{m6}}$$

$$\frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4} = \frac{I_6}{I_4} = \frac{I_{m6}}{I_{m4}}$$

$$\boxed{\left(\frac{w}{c}\right)_f = 14} \quad \text{we know}$$

$$g_m = \sqrt{\mu_p (C_{ox} \left(\frac{W}{L}\right) 2 \bar{V}_D)}$$

$$I_{mf} = 129.61 \mu$$

$$\begin{aligned} \left(\frac{w}{c}\right)_6 &= \frac{g_{m6}}{g_{m4}} \left(\frac{w}{c}\right)_4 \\ &= \frac{1600}{29.61} \times 14 \end{aligned}$$


$$\left(\frac{\omega}{L}\right)_6 = 173$$

$$\frac{I_6}{I_4} = \frac{(W/L)_6}{(W/L)_4}$$

$$I_6 = \frac{(W/L)_6}{(W/L)_4} \times I_4 = \frac{174 \times 10}{14}$$

$$I_6 = 124.28$$

$$I_6 = 125 \mu A$$

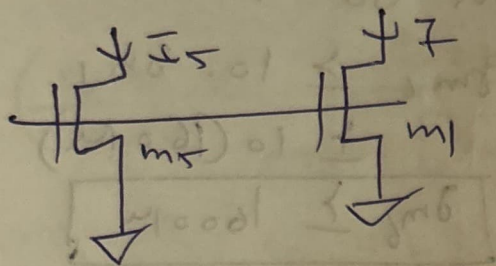

$$\frac{I_7}{I_5} = \frac{(W/L)_7}{(W/L)_5}$$

$$\left(\frac{W}{L}\right)_7 = \frac{I_7}{I_5} \cdot \left(\frac{W}{L}\right)_5$$

$$= \frac{125 \times 12}{20}$$

$$\left(\frac{W}{L}\right)_7 = 75$$

$$V_{thp} = -295.68m$$

$$V_{thn} \rightarrow 184.71m$$

$$I_{CMP} = 0.8$$

$$M3 \rightarrow -295.68m$$

$$I_{CMP} = 1.6$$

$$V_{thn} \rightarrow 22.947m$$

$$V_{thn} \rightarrow 120.765m$$

$$\beta_{eff} \rightarrow 300.632 \mu$$

$$\beta_{a eff} = 300.632 \mu$$

$$V_{thp} \rightarrow 160.606m$$

$$\beta_{a eff} = 142.924 \mu$$